

## Application Hints for external Oscillator Circuitry

### Topics:

- influences of the oscillator circuitry
- external oscillator circuitry for measurements of fundamental crystals
- measurement characteristics for the drive level
- definition of the oscillator start time
- application hints for the fine tuning
- effect of circuit composition when tuning some dedicated parameters
- appendix (measurement protocols of the SAB 80C517A, ES-LA)




### Influences of the Oscillator Circuitry

- components of the external circuitry
- stray capacitances and inductances
- crystal parameters
- board layout
- power supply rise time
- power supply quality
- temperature

Because of the above influences, Siemens as microcontroller manufacturer cannot give assured characteristics for the external oscillator circuitry . Therefore only recommendations can be given. The customer must proof in his application, whether his used external components for the oscillator circuitry correspond to his given demands.


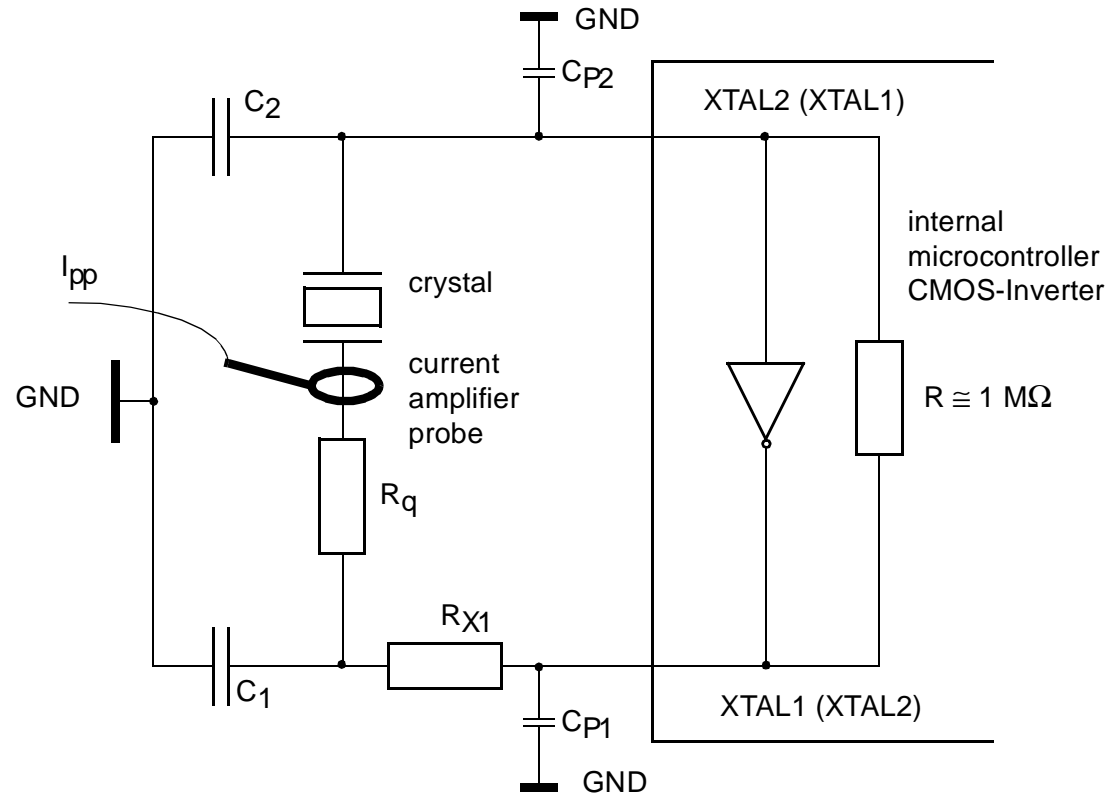
### External Oscillator Circuitry for Measurements of fundamental Crystals



- $C_1/C_2$  ... capacitors which are parts of the load capacitance  $C_L$
- $C_{P1}/C_{P2}$  ... probe capacitance; probes are used for measuring XTAL1/2 amplitudes and oscillation start time  $t_a$
- $I_{pp}$  ... measured drive current with current amplifier
- $R_{X1}$  ... resistor is used for optional controlling of the drive current
- $R_q$  ... resistor is used for checking the quality of the oscillation start up after power on (oscillation allowance)
- GND ... ground connection should be as close as possible to the controller GND pins (nearby XTAL pins)

### External Oscillator Circuitry



### Measurement Characteristics for the Drive Level

Drive Level: 
$$D_L = I^2 \times R_L$$

Drive Current: 
$$I = \frac{I_{pp}}{2 \times \sqrt{2}} \quad (\text{for sine waveform})$$

Transformed equivalent series resistance with load capacitances:

$$R_L = R_1 \times \left( 1 + \frac{C_0}{C_L} \right)^2$$

Load Capacitance: 
$$C_L = \frac{C_{X1} \times C_{X2}}{C_{X1} + C_{X2}} + C_S \quad \text{with:} \quad \begin{aligned} C_{X1} &= C_1 + C_{P1} \\ C_{X2} &= C_2 + C_{P2} \end{aligned}$$

- R<sub>1</sub> ... equivalent series resistance (see spec. from osc. crystal; typ. ≅ 50 Ω for crystals in the range from 8 to 20 MHz)
- C<sub>0</sub> ... shunt capacitance (see specification of oscillator crystal; ≅ 5 pF)
- C<sub>1</sub>/C<sub>2</sub> ... capacitors connected from ground to XTAL1/XTAL2 (C<sub>1</sub>/C<sub>2</sub> should not be smaller than C<sub>0</sub>)
- C<sub>P1</sub>/C<sub>P2</sub> ... probe capacitance; active probes ≅ 1 - 2 pF; passive probes 10 -15 pF
- C<sub>S</sub> ... stray capacitance, e.g. from the board layout; ≅ 0 - x pF (≅ 2 pF for a two layer board)


### External Oscillator Circuitry


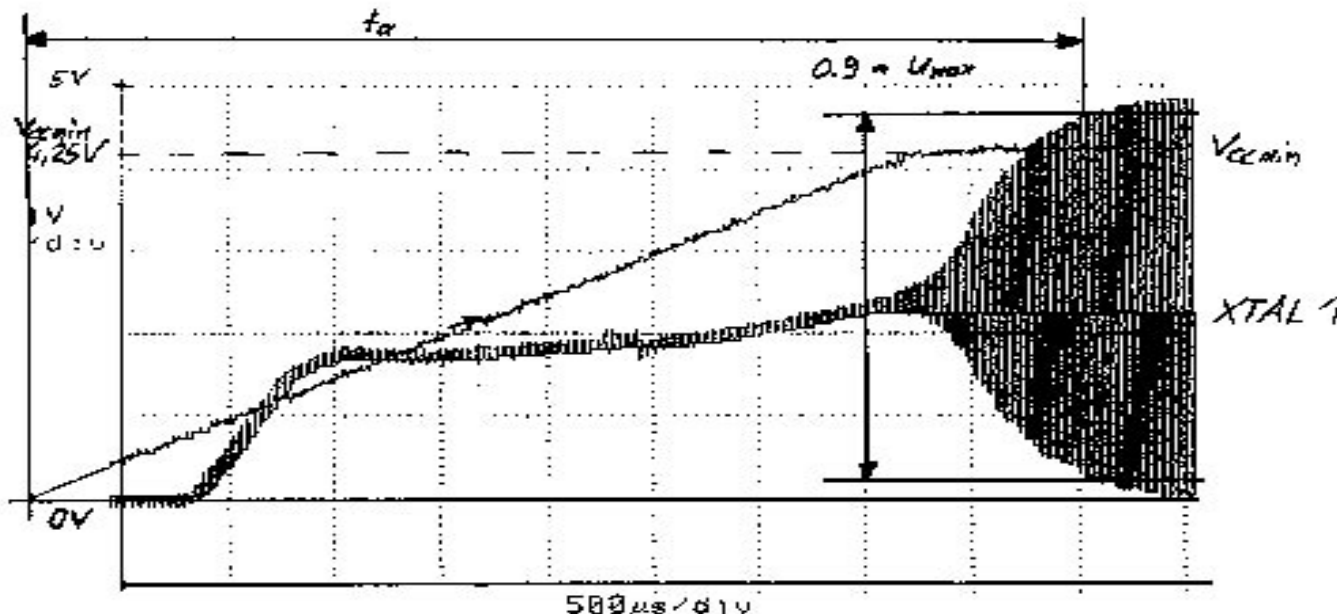
### Definition of the Oscillator Start Up Time $t_a$


The definition of the oscillator start up time is not a well defined value in the literature. On principal it depends from the power supply rise time  $dV_{cc}/dt$  at power on and the absolute  $V_{cc}$  level. For measurements the application specific power supply rise time  $dV_{cc}/dt$  and the  $V_{ccmin}$  level should be used. In the following two different definitions for  $t_a$  are shown with  $dV_{cc}/dt = 1 \text{ V/ms}$  and  $V_{ccmin} = 4.25 \text{ V}$ .

- Figure 1:  $t_a$  is measured between  $V_{cc} = 0 \text{ V}$  and the point where the oscillation reaches 90% of the maximum amplitude.


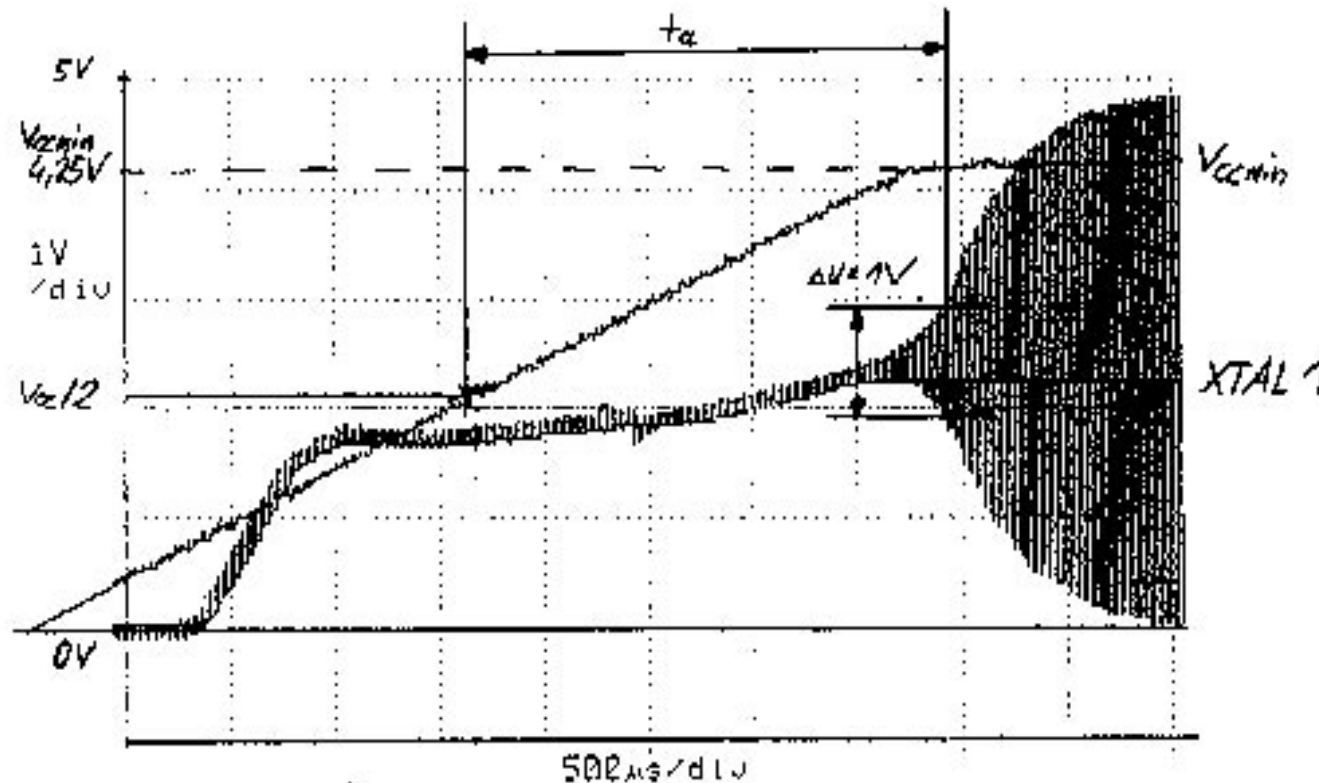
### Definition of the Oscillation Start Time $t_a$

- Figure 2:  $t_a$  is measured between  $V_{CC} = V_{CC}/2$  and the point where the oscillation reaches an maximum peak to peak value of 1V.



### Application Hints for the Fine Tuning

- Checking for Oscillation Allowance

Find out the maximum serial resistor  $R_q$ , where the oscillator circuit still starts up after power on. For this, vary  $R_q$  from low values to high values until the oscillator fails to start up. The last  $R_q$  value shows proper oscillation start up with its maximum value.

The quotient  $R_q/R_1$  is used for checking the oscillation allowance:

Demand:  $\frac{R_q}{R_1} \geq 5$  (the higher, the better)

Note:  $R_q$  is only used for checking the oscillation allowance and must be removed in the final application.  $R_q$  is often referred to as the negative resistance  $-R$  of the oscillator circuit.

- Drive current and life time:

For assuring the life time of the crystal unit, the used drive level in the application should be ten times lower than the specified maximum drive level for the oscillator crystal; e.g. with  $D_{LMAX} = 5 \text{ mW}$  the drive level in the application should be limited with  $R_{X1}$  to  $500 \mu\text{W}$ .

### Effect of circuit composition when tuning some dedicated parameters

#### influenced parameters

		I	XTAL1	ta	Rq/R1	DL=I <sup>2</sup> *RL		RL=
						Rq=0	Rq>0	R1*(1+C0/CL) <sup>2</sup>
variation of	C1=C2 ↑	↑	↓	↑	/	*	↓	↓
	C1=C2 ↓	↓	↑	↓	/	**	↑	↑

- \* (C1=C2) > 10 pF ---> ↑
- \* (C1=C2) < 10 pF ---> ↓
- \*\* (C1=C2) > 10 pF ---> ↓
- \*\* (C1=C2) < 10 pF ---> ↑

#### influenced parameters

		I	XTAL1	ta	Rq/R1	DL=I <sup>2</sup> *RL	RL=
							R1*(1+C0/CL) <sup>2</sup>
variation of	Rx1 ↑	↓	↓	↑	↓	↓	/
	Rx1 ↓	↑	↑	↓	↑	↑	/

- not influenced /
- rising ↑
- falling ↓

- DL drive level
- I drive current
- XTAL1 amplitude of oscillation at XTAL1 pin
- ta oscillation start up time
- Rq/R1 used for checking the oscillation allowance
- RL transformed equivalent series resistance





### Effect of circuit composition when tuning some dedicated parameters

#### influenced parameters

		I	XTAL1	ta	Rq/R1	DL=I <sup>2</sup> *RL	RL= R1*(1+C0/CL) <sup>2</sup>
variation of	Rq ↑	↓	↓	↑	/	↓	/
	Rq ↓	↑	↑	↓	/	↑	/

#### influenced parameters

		I	XTAL1	ta	Rq/R1	DL=I <sup>2</sup> *RL	RL= R1*(1+C0/CL) <sup>2</sup>
variation of	Vcc ↑	↑	↑	↓	↑	↑	/
	Vcc ↓	↓	↓	↑	↓	↓	/

not influenced /  
 rising ↑  
 falling ↓

DL drive level  
 I drive current  
 XTAL1 amplitude of oscillation at XTAL1 pin  
 ta oscillation start up time  
 Rq/R1 used for checking the oscillation allowance  
 RL transformed equivalent series resistance

