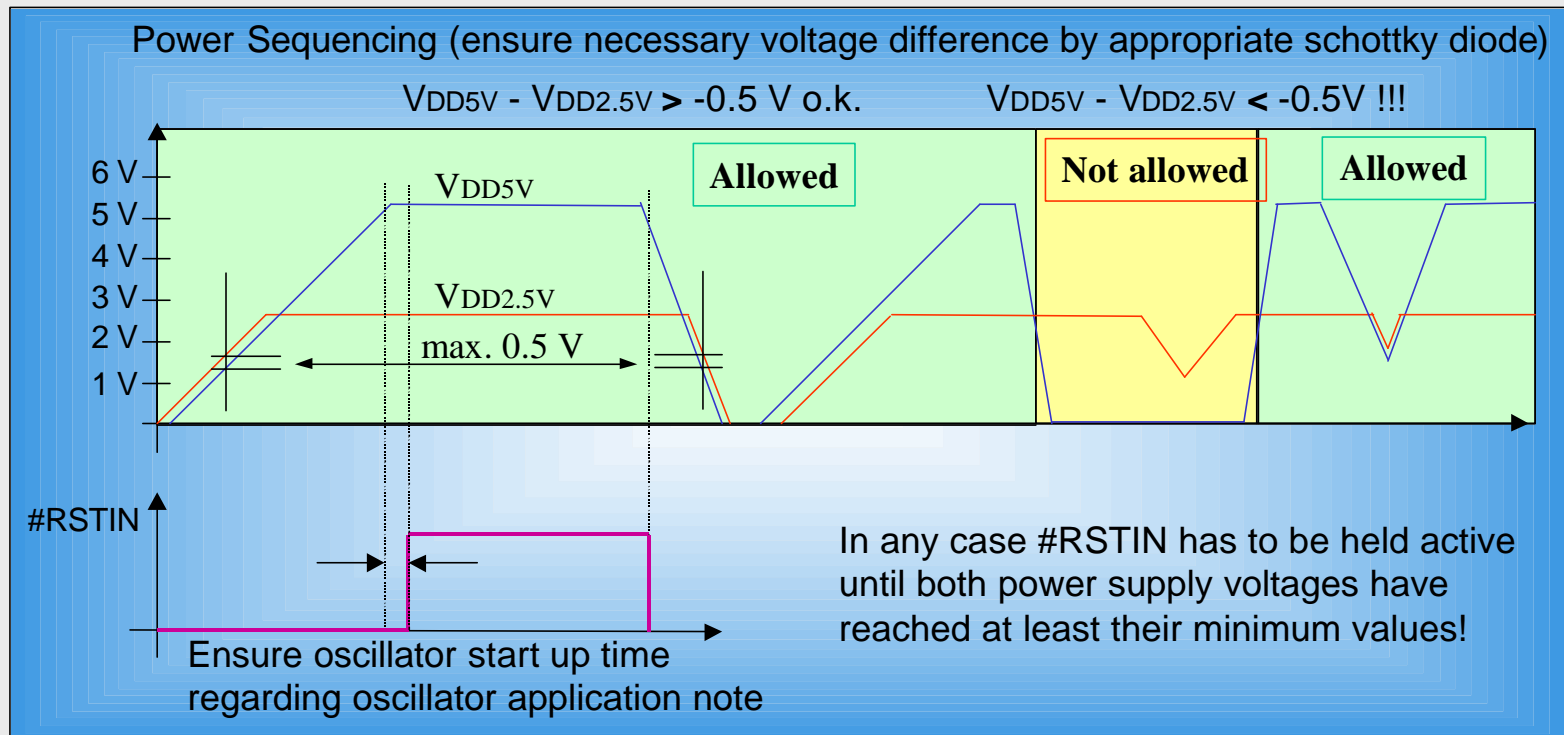


Power Supply

- Dual voltage power supply required.
 - 5V for I/O, ADC, and Port structures (V_{DD5V})
 - 2.5V for internal core, and XTAL ($V_{DD2.5V}$)
 - It must be ensured that $V_{DD5V} - V_{DD2.5V}$ is never less than -0.5V




Power Supply

■ Reset Circuit

- Reset must be held low until both power supplies have reached at least their respective minimum operating voltages:
 - ◆ $V_{ddi} = 2.4V$
 - ◆ $V_{ddp} = 4.5V$
- Reset must remain low for at least 100ns to be reliably detected (from a XTAL running state)
- Reset should remain low for at least 50ms to allow XTAL and PLL start-up (from a XTAL not running state)
- RSTIN pin no longer has a built in pull up resistor, so needs to be biased externally. (Contrary to existing documentation)


Power Supply

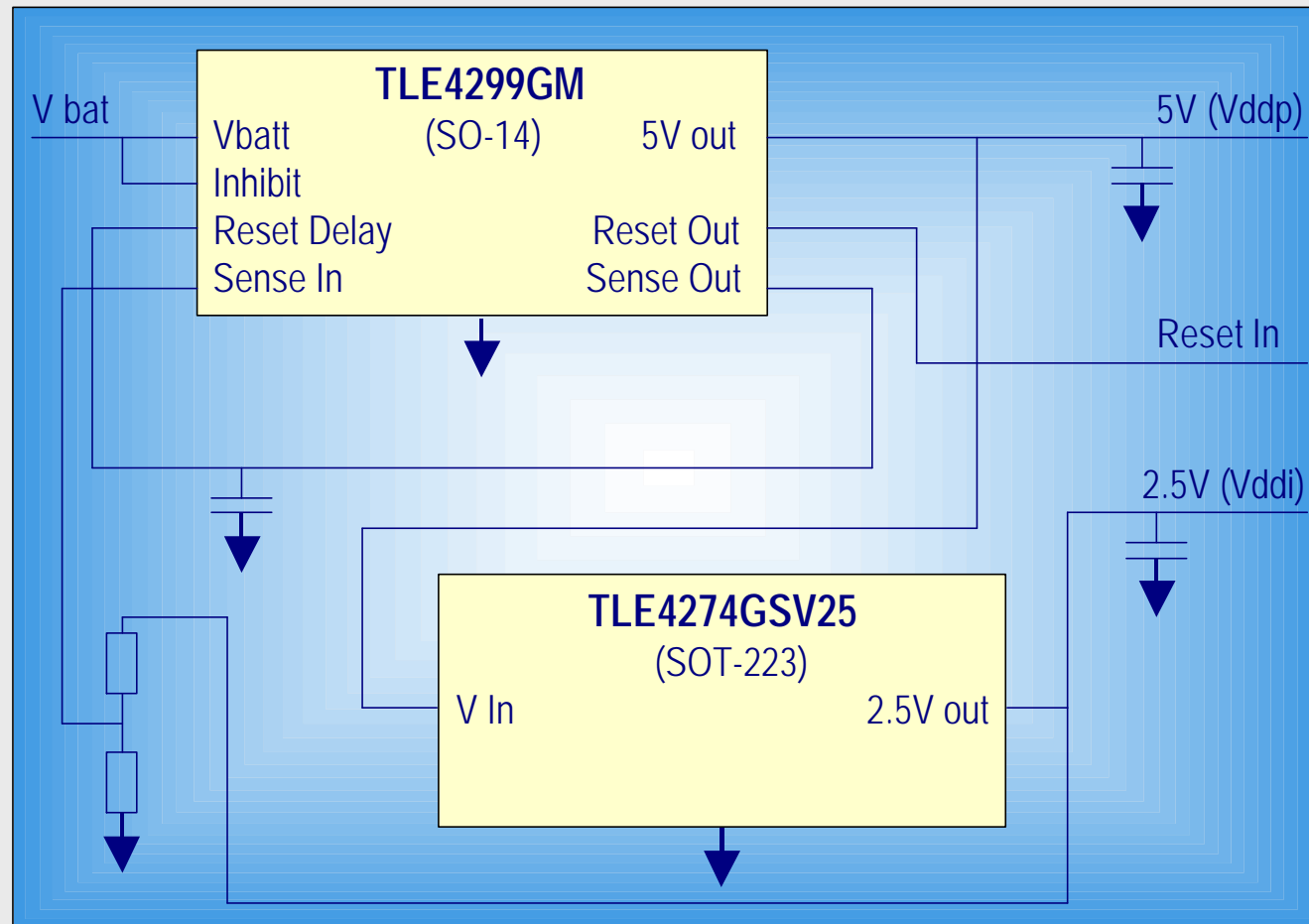■ Voltage Regulator and Reset Circuit Discrete Realisation



Voltage regulator TLE7469

 - Output 5V/220mA & 2.6V/200mA
- Ultra low quiescent current <math><55\mu\text{A}</math>
- Stable with some 100nF
- Active power sequencing
- Window watchdog
- Output reverse current sink
- Early warning comparator
- Inhibit input
- Very low drop voltage
- P-DSO-12



Voltage regulator TLE7469

- Voltage Regulator and Reset Circuit Integrated Solution
 - Includes a windowed watchdog

